

Instrumentation Amplifier

Amaan Rahman
The Cooper Union
ECE-444: Bio-instrumentation

March 7, 2022

1 Abstract

The instrumentation amplifier is 2-stage amplifier; the former stage consists of 2 differential operation amplifiers configured as buffer amplifiers, and the latter stage consists of a unity gain amplifier. The advantages of this amplifier topology are high open loop gain and high Common-Mode-Rejection-Ratio (CMMR). Thus, the instrumentation amplifier is practical in scenarios where a differential signal is small and further amplification is required.

2 Introduction

An LTSpice simulation schematic has been setup, as can be seen in (FIGURE). The physical circuit has been built accordingly to the topology structure in (FIGURE).

The gain of the circuit can be derived as follows:

Let v_{o_i} represent the output voltages of each respective operational amplifier, and v_x , v_y be the input volatges of the unity gain buffer.

$$\begin{aligned}\Delta v_{in} &= v_{+in} - v_{-in} \\ \left. \begin{aligned} \frac{v_{out} - v_y}{R} &= \frac{v_y - v_{o1}}{R} \\ \frac{v_{out} - v_x}{R} &= \frac{v_{o2} - v_x}{R} \end{aligned} \right\} \implies v_{out} = v_{o2} - v_{o1} \because \{v_x = v_y\} \\ \frac{v_{o2} - v_{o1}}{2R_2 + R_1} &= \frac{\Delta v_{in}}{R_1} \\ \frac{v_{out}}{2R_2 + R_1} &= \frac{\Delta v_{in}}{R_1} \\ A_v = \frac{v_{out}}{v_{in}} &= 1 + \frac{2R_2}{R_1}\end{aligned}$$

3 Procedure

Components:

- 3 411 Operational amplifiers
- $R_2 : 250k\Omega$
- $R_1 : 500\Omega$
- $R : 1k\Omega$

4 Results

5 Discussion

According to (FIGURE OF EXPERIMENTAL GAIN PLOT), the corner frequency is around 2kHz; however, in simulation, (FIGURE OF SIM GAIN PLOT), the corner frequency is around 1kHz. This 1kHz difference in the corner frequency could be due to the propagated delays of capturing the gain at each frequency in the frequency response through a script to automate the frequency response, in courtesy of Richard Lee. It could also be due to the resistance values and the effect of parasitic capacitances of the operational amplifier.

There was difficulty in figuring out where the corner frequency is derived from exactly, but through prolonged experimentation and simulations, manipulating R_2 and R_1 ratio such that gain is very large ($\sim 500 \frac{V}{V}$) yields in decreasing the corner frequency such that the bandwidth decreases dramatically.

Another difficulty was generating the frequency response of the instrumentation amplifier without tabulating oscilloscope data by hand. Due to never using a spectrum analyzer before, it took time to figure it out. Nonetheless, all signals were visible at various frequencies. If the center frequency matches the frequency of the output signal frequency, a main lobe is observed with a gain (dB) that matches the expected gain of the instrumentation amplifier. However, a frequency sweep was required to generate the appropriate gain bode plot of the instrumentation amplifier, and that functionality could not be discovered as of yet.

6 Appendix: Simulations